

Electricity


Worksheet


NCF and/or NCERT Learning Outcomes:


• To assess the understanding of basic electrical circuits.


Why should you learn this?

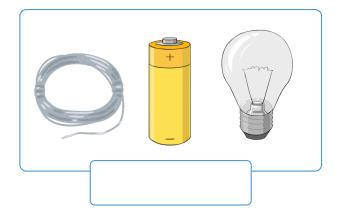- Solving this worksheet helps you to self-assess your learnings and identify problem areas.
- Below are four images. Which of the combination of components shown in the pictures will make the bulb glow? Mark
 or
 in the space below each picture.



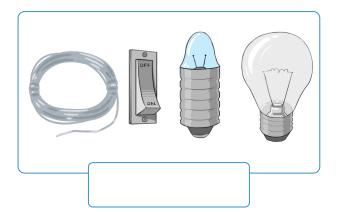

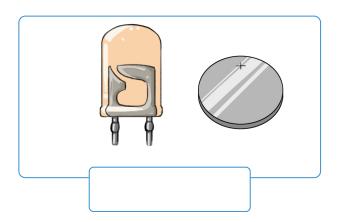


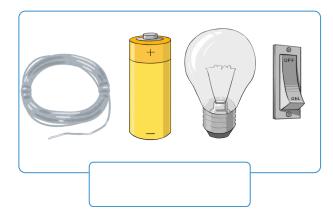







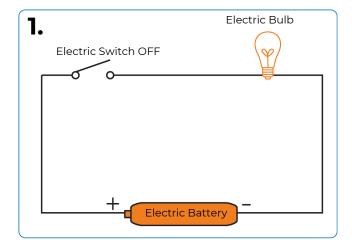
Look at the 4 electrical circuits shown below carefully. In which of them will the bulb glow? Is it an open circuit or a closed circuit?



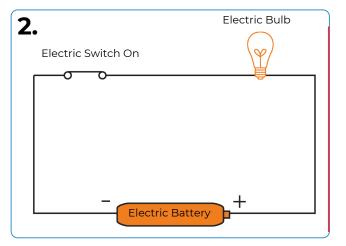

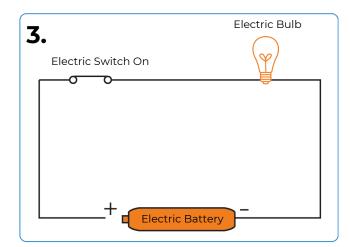

Answer:

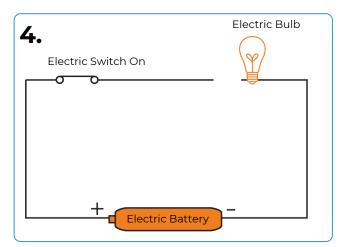



3 Match the given components with their correct symbols.


Components	Symbols
+	
	- - - - -
© OFF	
OFF ON O	





Electric Bulb

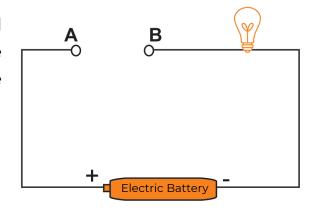Which of the objects listed below will make the bulb glow when they are placed between points A and B in the given circuit? Why?




Sr. No.	Object	Will the bulb glow?	Why?
1	Pencil		
2	Nail		
3	Bicycle spoke		
4	Comb		
5	Paper		
6	A piece of wood		



Draw an electrical circuit diagram in the box/in your component symbols of a switch, a wire, a bulb, a symbol of a switch of the cell is connected, and the wires are properly not lighting up. What could be the reasons for the cell is consecuted to the could be the reasons for the cell is connected.	easons		
The cell is connected, and the wires are properly not lighting up. What could be the reasons for t			
The cell is connected, and the wires are properly not lighting up. What could be the reasons for t			
The cell is connected, and the wires are properly not lighting up. What could be the reasons for t			
The cell is connected, and the wires are properly not lighting up. What could be the reasons for t	+	· <u> </u> +	-1-+
The cell is connected, and the wires are properly not lighting up. What could be the reasons for t			
The cell is connected, and the wires are properly not lighting up. What could be the reasons for t			
The cell is connected, and the wires are properly not lighting up. What could be the reasons for t	our no	tebook	k using
not lighting up. What could be the reasons for t			_
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t		•••••	
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t			
not lighting up. What could be the reasons for t	y attach	ned, bu	it the bulb
Answer:			•
	_		
	_	Land	



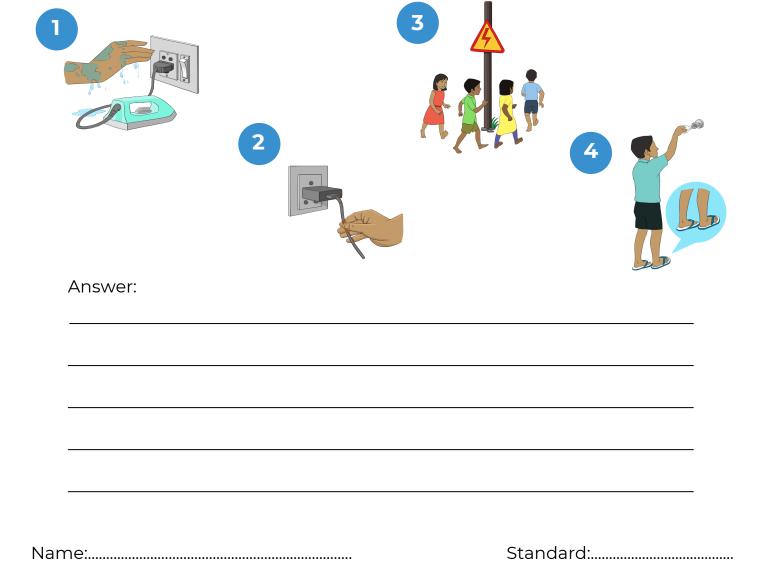8 In the pictures below, children are performing some activities. Are the activities safe? Explain with a reason.



This resource is aligned with competencies outlined in the National Curriculum Framework (NCF) and National Council of Educational Research and Training (NCERT). For more information write to digital.repository@pratham.org.